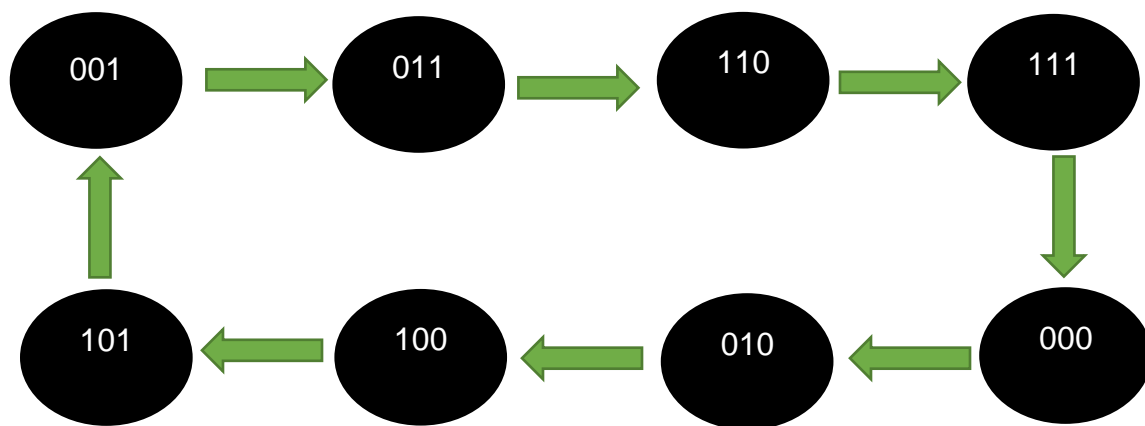


## Experiment Design

Design the synchronous sequential counter circuit that counts periodically as  $1 \rightarrow 3 \rightarrow 6 \rightarrow 7 \rightarrow 0 \rightarrow 2 \rightarrow 4 \rightarrow 5 \rightarrow$  using T flip flop?

### 1. State Diagram:

A state diagram visually represents a system's states and transitions triggered by specific events or conditions.



### 2. State Table:

A State Table is a tabular representation of a sequential circuit that shows all possible states, inputs, next states, and outputs.

Present State			Next State			Flip-Flops Input		
Q <sub>C</sub> (n)	Q <sub>B</sub> (n)	Q <sub>A</sub> (n)	Q <sub>C</sub> (n+1)	Q <sub>B</sub> (n+1)	Q <sub>A</sub> (n+1)	T <sub>C</sub>	T <sub>B</sub>	T <sub>A</sub>
0	0	1	0	1	1	0	1	0
0	1	1	1	1	0	1	0	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1
0	0	0	0	1	0	0	1	0
0	1	0	1	0	0	1	1	0
1	0	0	1	0	1	0	0	1
1	0	1	0	0	1	1	0	0

### 3. Excitation Table of T Flip-Flop:

Q(n)	Q(n+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

### 4. Simplified Boolean Function of Flip Flop Input:

For  $T_A$ :

$Q_B Q_A$ $Q_C$	00	01	11	10
0			1	
1	1		1	1

Equation 1:

$$T_A = Q_B Q_A + Q_C Q'_A \dots \dots \dots (1)$$

For  $T_B$ :

$Q_B Q_A$ $Q_C$	00	01	11	10
0	1	1		1
1			1	

Equation 2:

$$T_A = Q'_C Q'_B + Q'_C Q'_A + Q_C Q_B Q_A \dots \dots \dots (2)$$

For T<sub>C</sub>:

Q <sub>B</sub> Q <sub>A</sub>	00	01	11	10
Q <sub>C</sub> 0			1	1
Q <sub>C</sub> 1		1	1	

Equation 3:

$$T_A = Q'_C Q_B + Q_C Q_A \dots \dots \dots (3)$$

## 5. Schematic Diagram From Circuitverse:

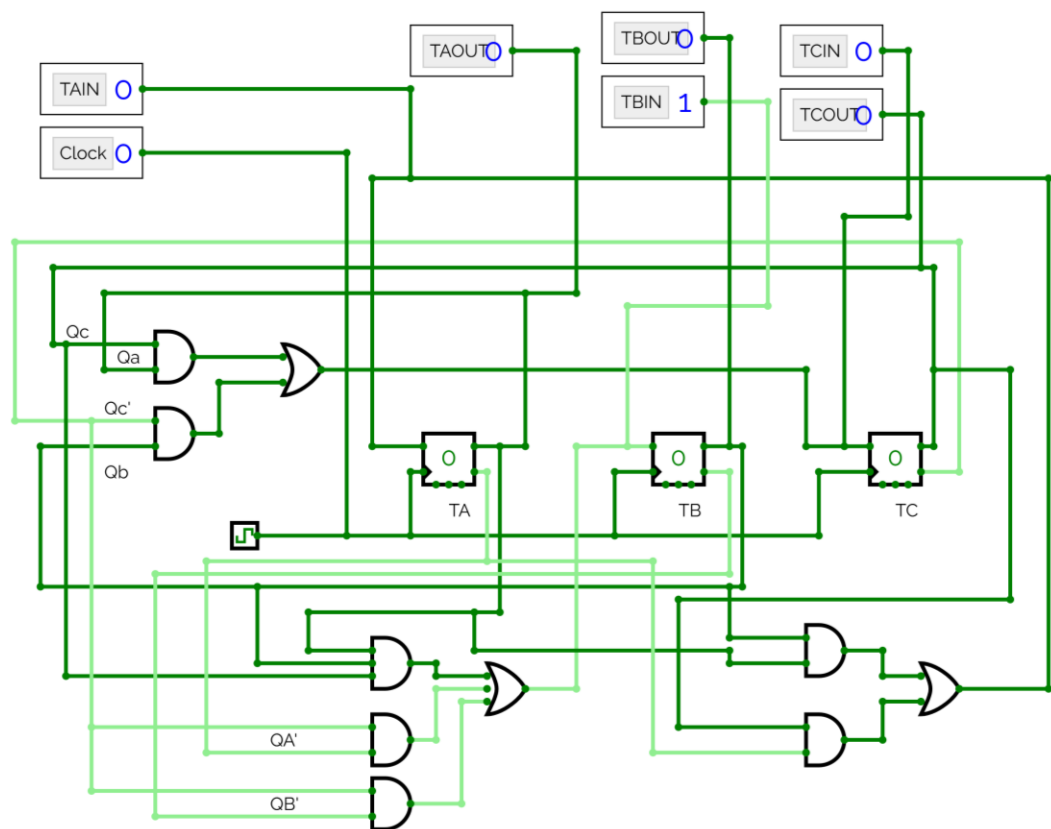


Figure 1: Schematic Diagram

## 6. Timing Diagram:

